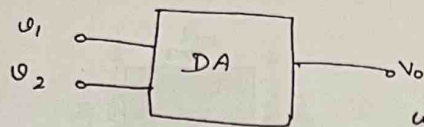


Differential Amplifier



$$v_0 = A_{v_o}(v_1 - v_2)$$

where A_{v_o} is called open loop gain

We define the differential mode input voltage as


$$v_d = v_1 - v_2$$

and common mode input voltage as

$$v_{cm} = \frac{v_1 + v_2}{2}$$

$$v_0 = A_d v_d + A_{cm} v_{cm}$$

Differential Mode

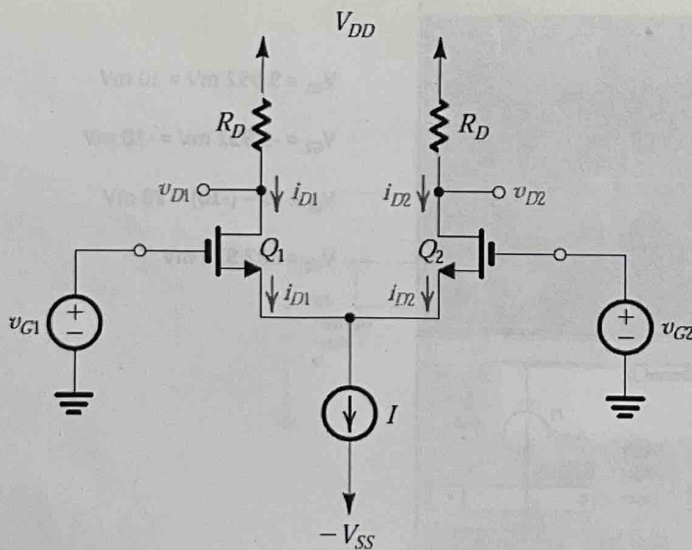

Output:

Single ended output = $v_{D2} = v_{od}$


Double ended output = $v_{D1} - v_{D2} = v_{od}$

Input = $v_{G1} - v_{G2} = v_{id}$


A_d = Differential mode gain

$$A_d = v_{od} / v_{id}$$

Differential Mode

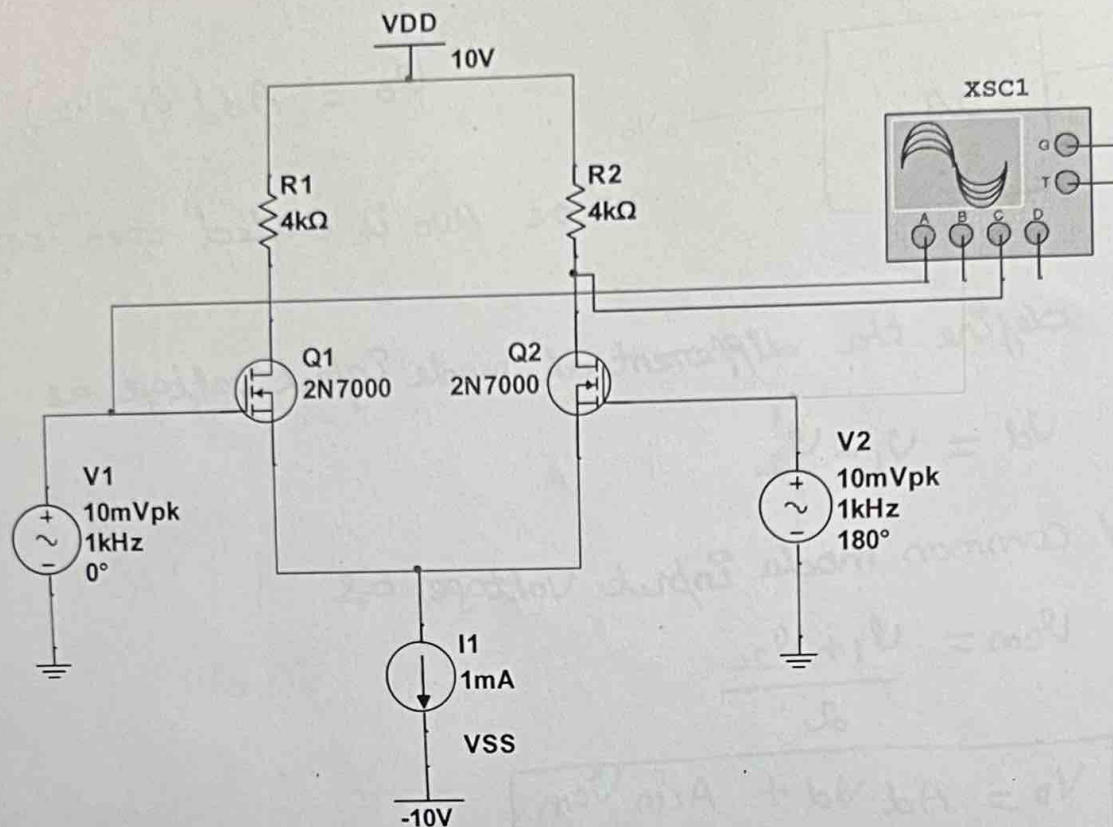

Common mode operation

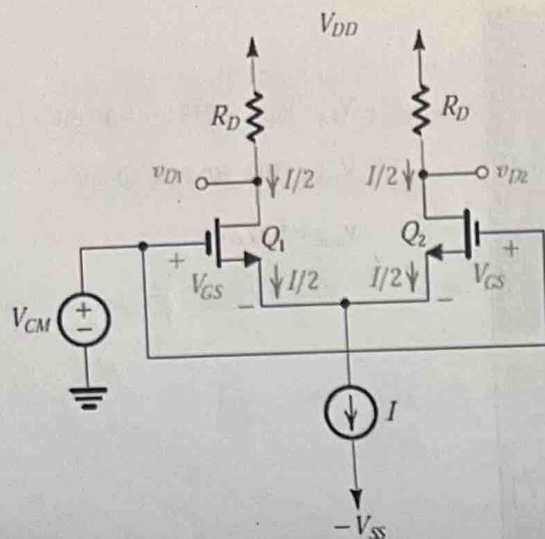

Output:

Single ended output = $V_{D2} = V_{out}$

Double ended output = $V_{D1} - V_{D2} = V_{out}$

Input = $(V_{G1} + V_{G2})/2 = V_{cm}$


A_{cm} = Common mode gain

$A_{cm} = V_{out} / V_{cm}$

Common Mode Rejection Ratio

$CMRR = 20 \log |A_d/A_{cm}| \text{ dB}$

Common Mode Response

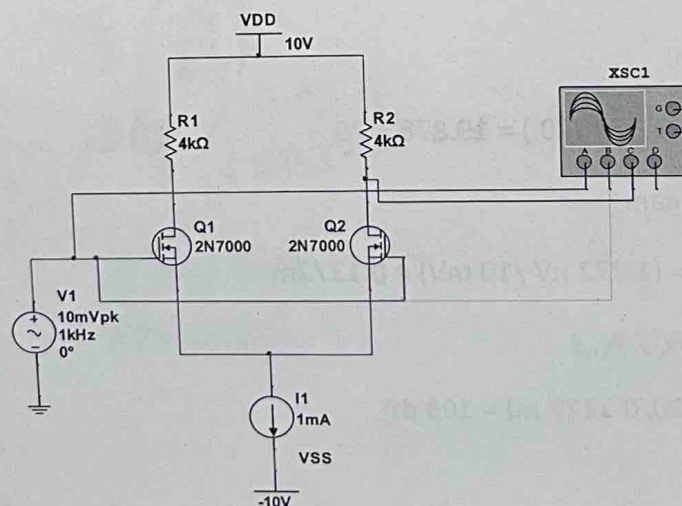

Task 4

- Design a differential amplifier with a load resistance of 10k, constant current source of 2 mA and supply voltage of $\pm 15V$.
- Determine the A_d , A_{cm} and CMRR.

Sol: $V_{od} = 358.4 \text{ mV}$, $V_i = 10 \text{ mV}$

$$\therefore A_d = \frac{V_{od}}{2V_i} = \frac{358.4}{20} = 17.92$$



$$V_{ocm} = 3.209 \text{ } \mu\text{V} \\ = 0.003209 \text{ mV}$$



$$A_{cm} = \frac{0.003209}{10} = 0.0003209$$

$$\therefore \text{CMRR} = 20 \log \left(\frac{A_d}{A_{cm}} \right) \\ = 20 \log \left(\frac{17.92}{0.0003209} \right)$$

$$= 20 \times 4.747$$

$$= 94.94 \text{ dB}$$

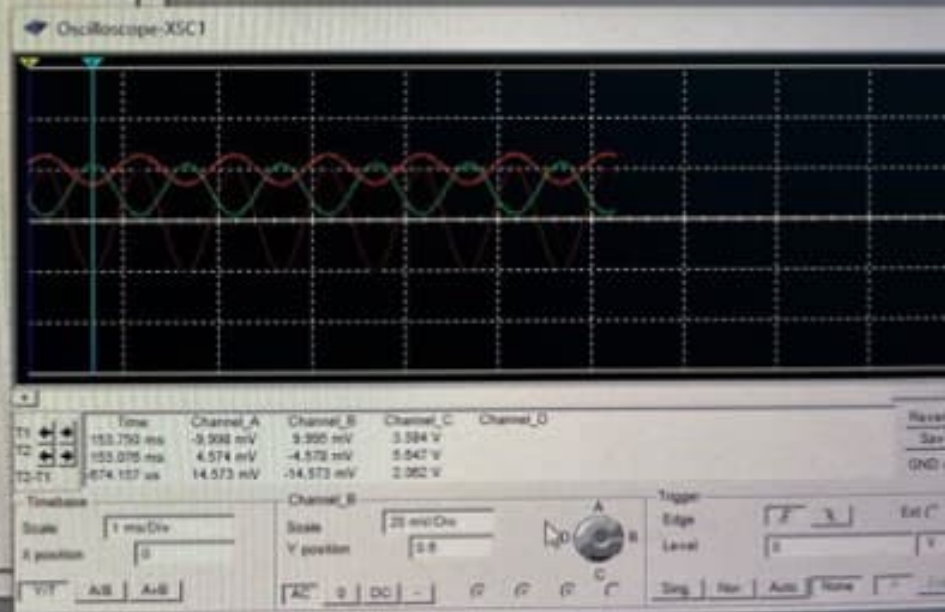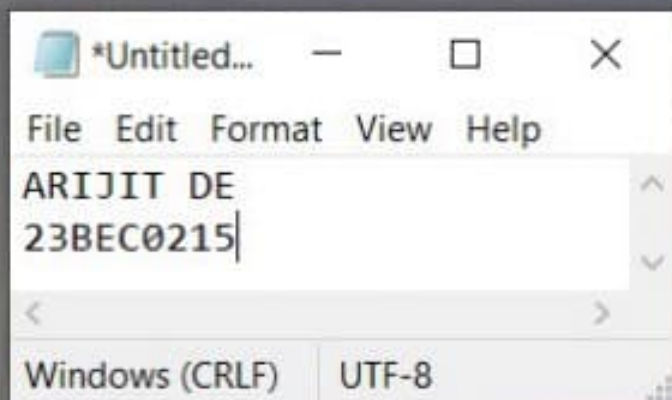

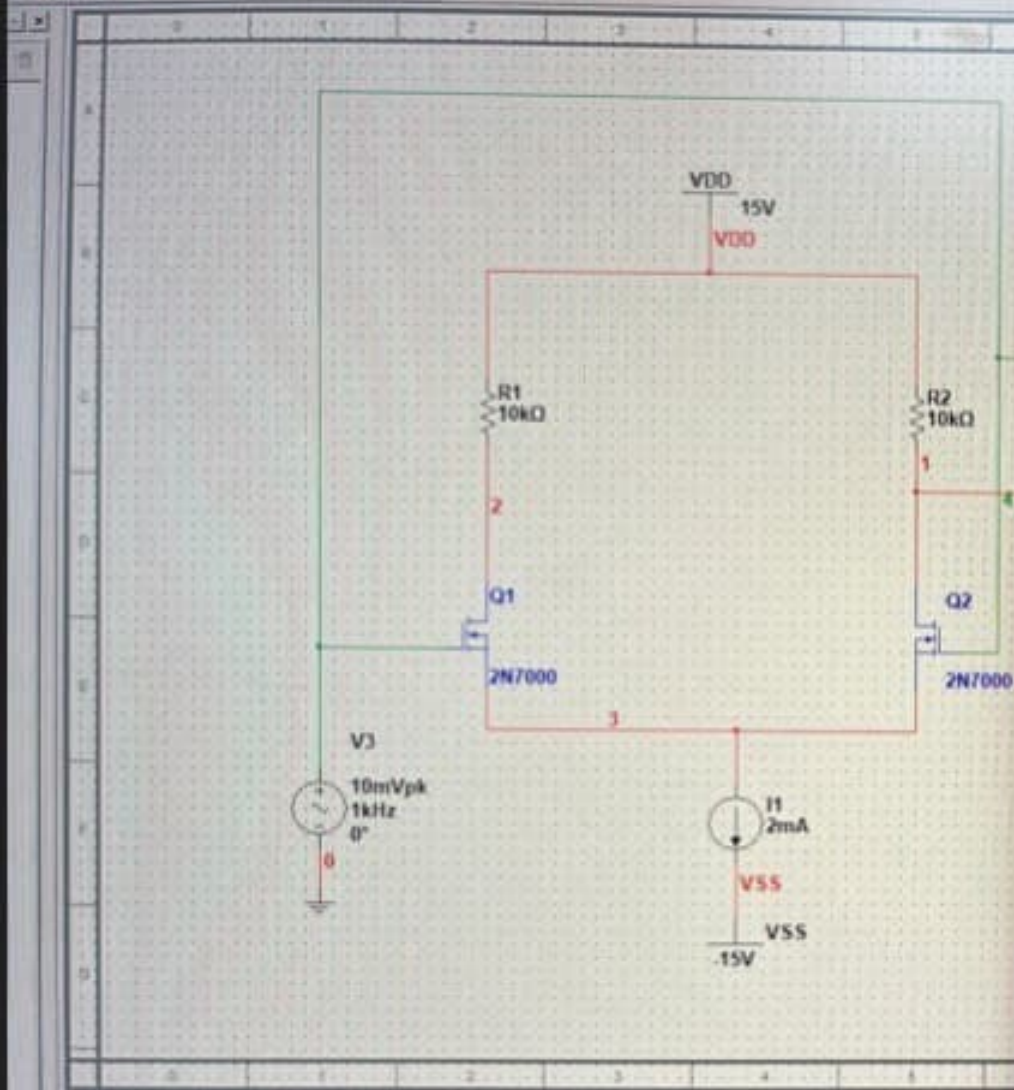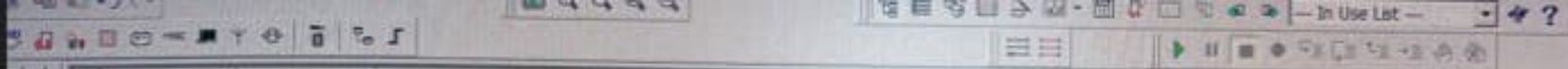

*Untitled... — □ ×

File Edit Format View Help

ARIJIT DE
23BEC0215

< >

Windows (CRLF) UTF-8

